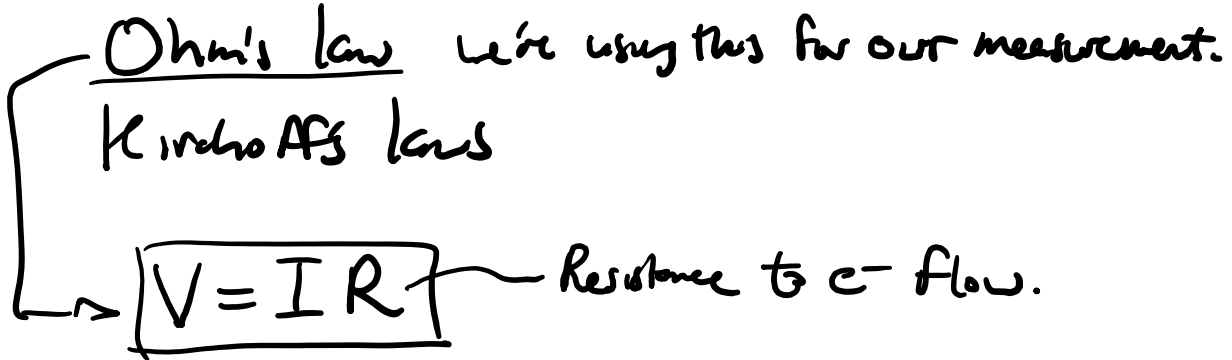


# Analogy Electronics I: resistors & V-dividers

Tuesday, September 15, 2020 8:18 PM

pg. 1-44 in Horowitz & Hill, The Art of Electronics.

2 Fundamental laws:



Voltage / potential  
flow of  $e^-$

Analogy to hydrodynamics:


$$H = J \cdot R$$

↑ hydrostatic pressure    ↑ fluid flow    ↓ Hydrodynamic resistance

"A Volt pushes an Amp through an Ohm."  
— potential energy / unit charge.

# Voltage is measured relative to a reference potential.

"Ohmic" vs. "non-Ohmic" behavior

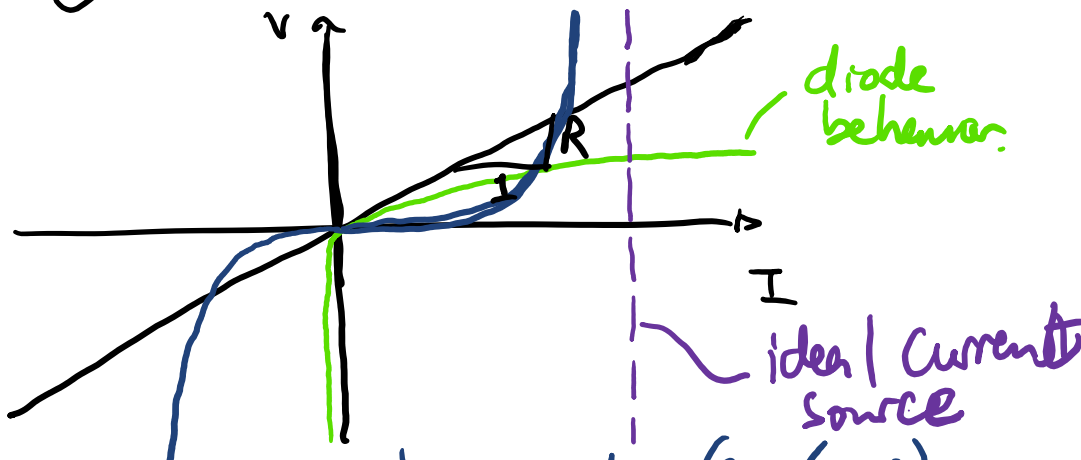



Power:  $P = IV = I^2R$


$I$ : current, charge/time  $\leftarrow$  Ohm's law.

$V$ : Work or energy/charge

$$[IV] \frac{\text{work}}{\text{time}} = \frac{\text{energy}}{\text{time}} = [P].$$


Kirchoff's laws:

I:

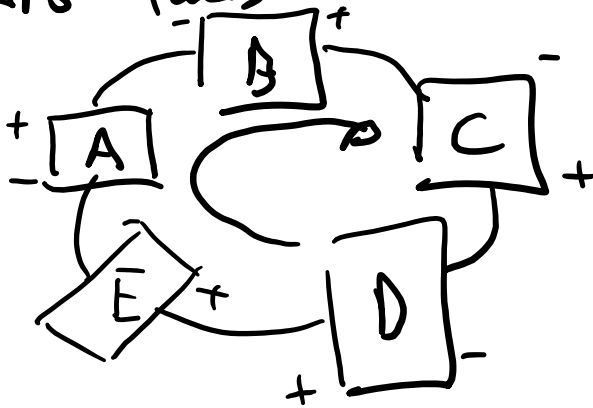


$\rightarrow$  Sum of voltages around a closed loop is 0.

II

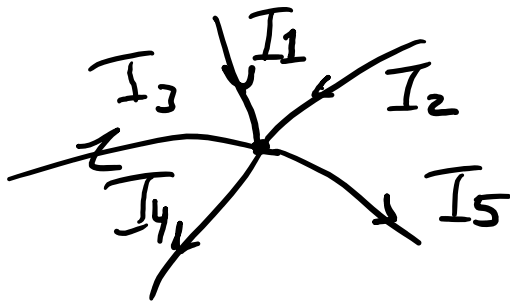

$\rightarrow$  Sum of the currents at a node is 0.

Example:

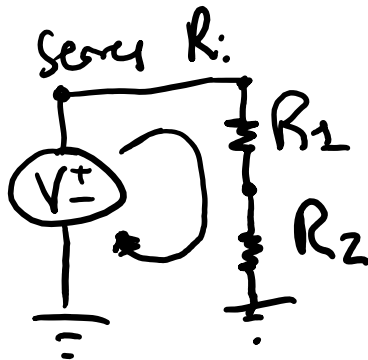

$$I_{\text{tot}} = I_1 = I_2 \text{ by K2.}$$


$$V_{\text{tot}} = V_1 + V_2 \text{ (K1)}$$

An eq. resistance:



$$V_{\text{tot}} = I_{\text{t}} R_{\text{eq}} = I_{\text{t}} R_1 + I_{\text{t}} R_2$$


1th eq. resistance.

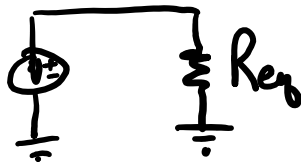

$$V_{tot} - I_{tot} R_{eq} = I_{tot} R_1 + I_{tot} R_2$$

$$\Rightarrow R_{eq} = R_1 + R_2.$$


parallel resistors:

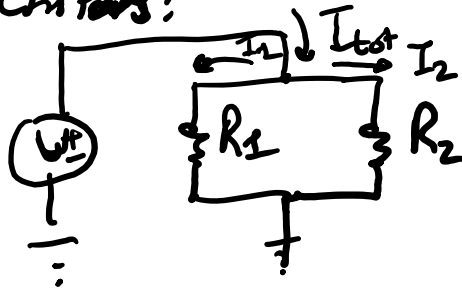

$$I_{tot} = I_1 + I_2 \quad (K2)$$

$$V_{tot} = V_1 = V_2 \quad (K1).$$

equivalent R:

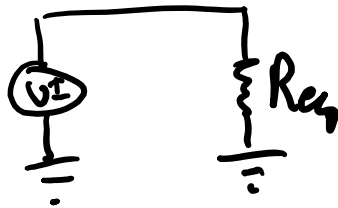

$$V_{tot} = I_{tot} R_{eq} = V_1 = V_2$$




$$I_{tot} R_{eq} = I_1 R_1 = I_2 R_2$$

$$I_{tot} = I_1 + I_2 \quad ; \quad I_1 = \frac{V}{R_1} \quad ; \quad I_2 = \frac{V}{R_2}$$

$$I_{tot} = \frac{V}{R_{eq}}$$



$$\frac{V}{R_{eq}} = \frac{V}{R_1} + \frac{V}{R_2} \Rightarrow R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

Consider these cases:

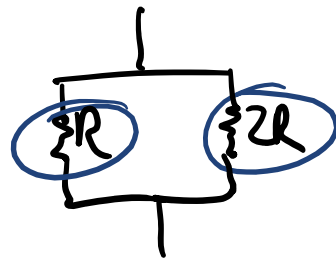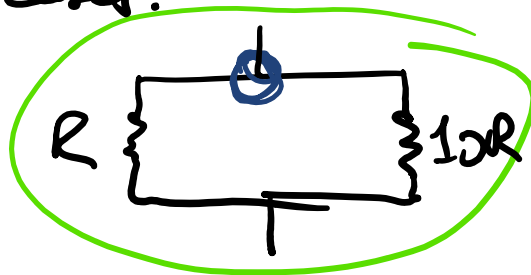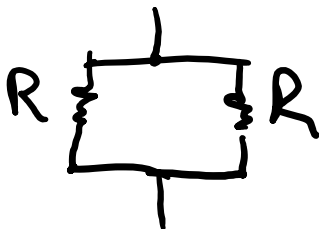


$$R \parallel R \Rightarrow R_{eq} = \frac{R^2}{2R} = \frac{R}{2}$$
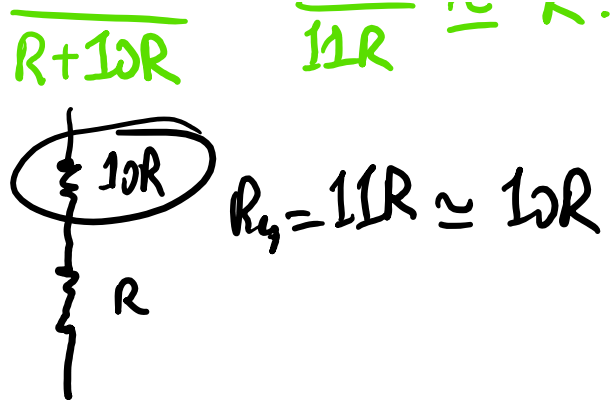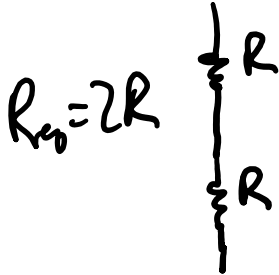
$$0 \parallel 10R \Rightarrow R_{eq} = 10R^2 - 10R^2, \quad 0$$



### V-divider (a device)

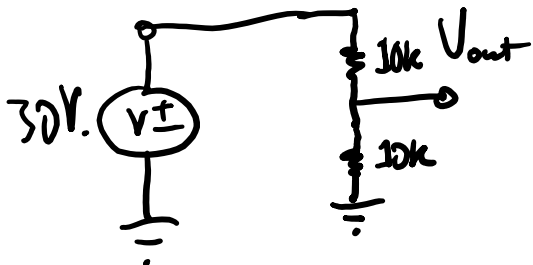

Solve for  $V_{out}$ :

$$I = \frac{V_{in}}{R_1 + R_2}; \quad V_{out} = IR_2$$

$$V_{out} = \frac{V_{in} R_2}{R_1 + R_2} = \frac{V_{in}}{2}$$

Using device?

