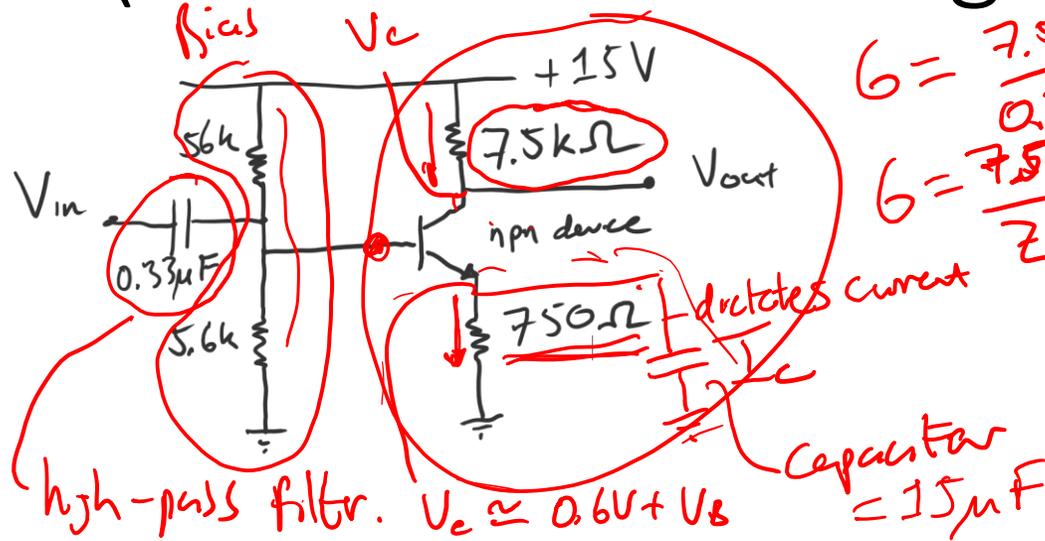


Week 4: Transistors cont'd – Ebers-Moll, differential amplifiers, toward an op-amp from discrete components

# Let's begin by revisiting the emitter amplifier (here with blocking cap and DC-offset)



$\beta = \frac{7.5k}{0.75k} @ D.C.$   
 $\beta = \frac{7.5k}{Z_e} @ A.C.: \text{can become v. large!}$

Recall property 4 of transistors, from last week:  $I_C = \beta I_B$

... but this breaks down when we ask too much of our transistor...

This brings us to a slightly modified (and more accurate) representation of the BJT: the Ebers-Moll model. Provided properties 1-3 are satisfied ( $V_C > V_E$ ;  $V_{BE} > 0.6$ ;  $I_C, I_B$  &  $V_{CE}$  below limit values):


$$I_C = I_S \left( e^{\frac{q V_{BE}}{kT}} - 1 \right)$$

Where  $I_S$  is the  $T$ -dependent saturation current of the transistor. Note that  $\frac{kT}{q} = V_T = 25 \text{ mV} @ \text{Room Temp.}$

Introduction of blocking cap enhances gain and introduces non-linear response of the amplifier

✗ Points for discussion on Piazza:

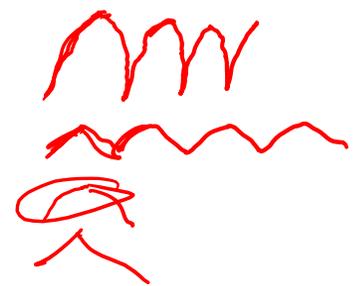
1. What is the input impedance for this amplifier, and why?
2. What is  $f_{3dB}$  for the emitter leg configuration including a 15 μF capacitor?




# How does Ebers-Moll alter our four properties of transistors?

Ebers-Moll implies the following four important quantities (see AoE § 2.10):

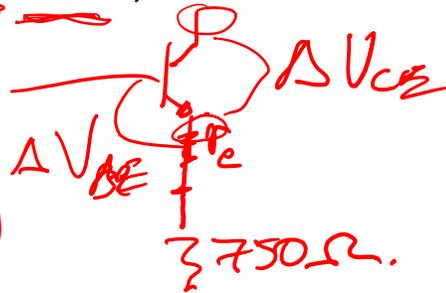1. We must now view our transistor as a trans-conductance device: it can drive currents in proportion to  $V_{BE}$ . With E-M, this implies a diode curve. From E-M relation, we can calculate the required increase in  $V_{BE}$  to generate a 10-fold increase in  $I_C$ :  $I_C = I_{C0} e^{\Delta V / 25mV}$ . At room temperature. This corresponds to an increase of 10x per  $\sim 60mV$  increase of  $V_{BE}$ .
2. Small-signal impedance into the emitter implies a 'little- $r_e$ ' – this resistance can be calculated by taking the derivative of  $V_{BE}$  with respect to  $I_C$ :  $r_e = \frac{V_T}{I_C} = \underline{25mV / I_C}$  ohms. Here,  $r_e$  acts like a series resistor with the emitter leg.
3.  $V_{BE}$  has a negative temperature coefficient (it decreases as  $T$  increases).
4. The Early effect:  $V_{BE}$  depends on  $V_{CE}$  as:  $\Delta V_{BE} = -\alpha \Delta V_{CE}$ , where  $\alpha$  is typically  $1e-4$ .



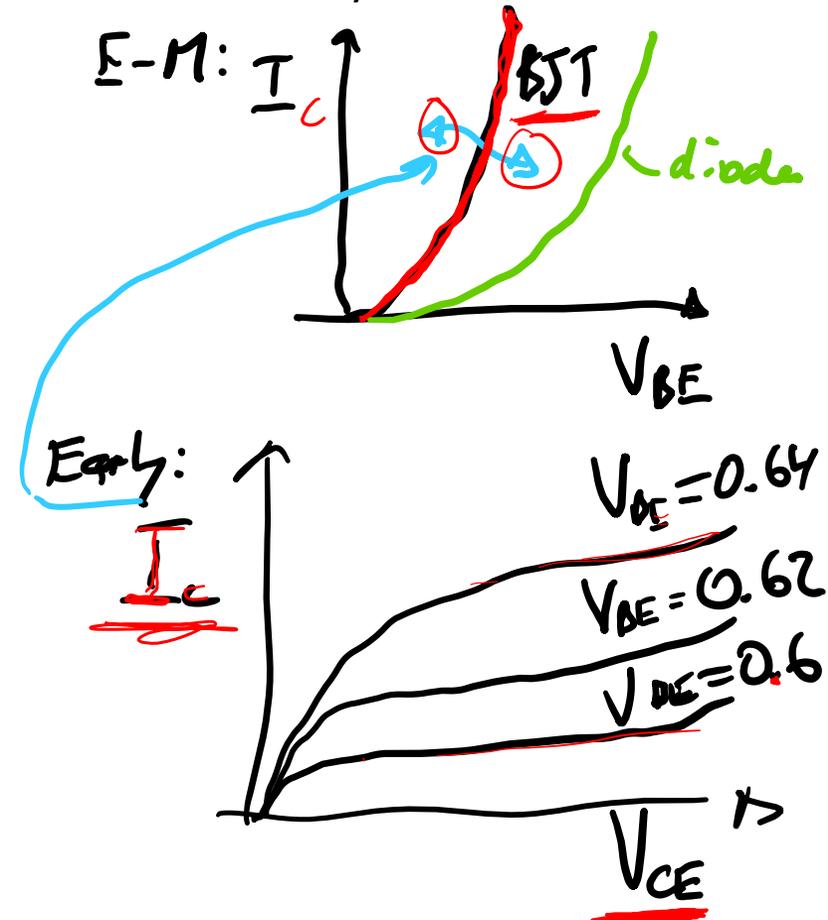
A graphical summary of Ebers-Moll and the Early Effect:



Points for discussion on Piazza:  
 Why does  $V_{BE}$  have a negative Temp. coefficient?  
 (Hint: it has to do with how  $I_S$  behaves)

An inelegant segue: The dreaded *common-mode*:  
how to handle a signal that is susceptible to  
ambient electrical noise?

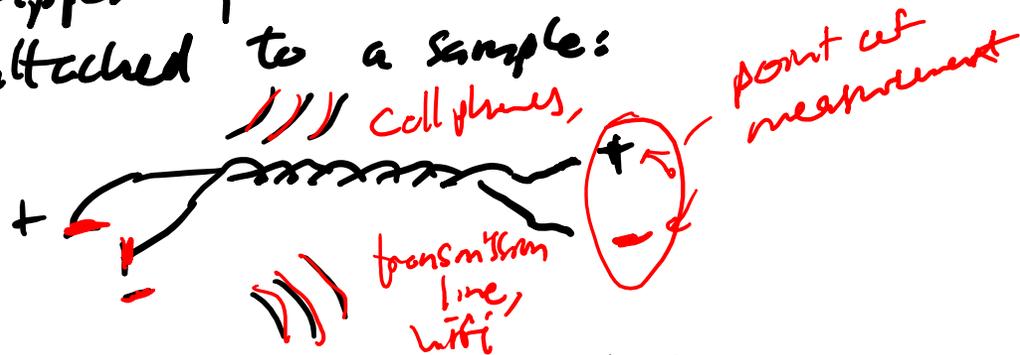Suppose you have a transducer  
attached to a sample:




And there is ambient electrical noise.

Note that both leads,  $+ \Delta -$   
carry this noise!


- you can easily see this from  
the 50 Hz signal carried  
on power lines.

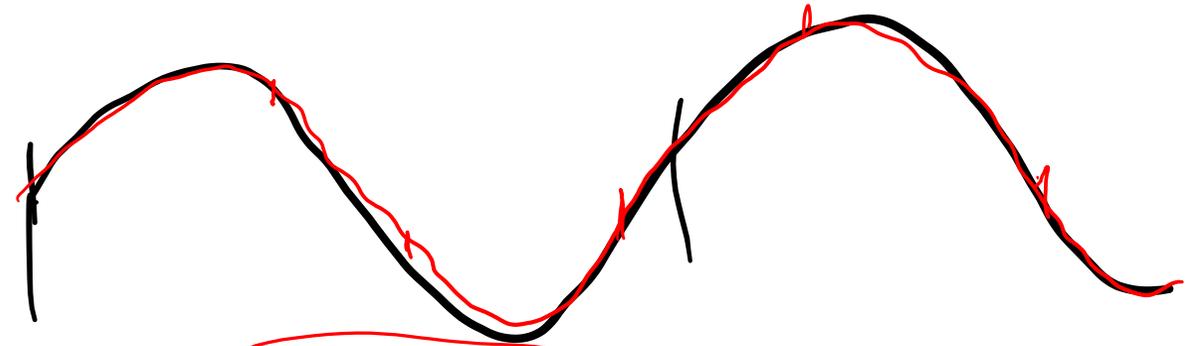Often, your signal will look  
like this:



$$\Delta T = \frac{1}{50}$$


While expecting this:

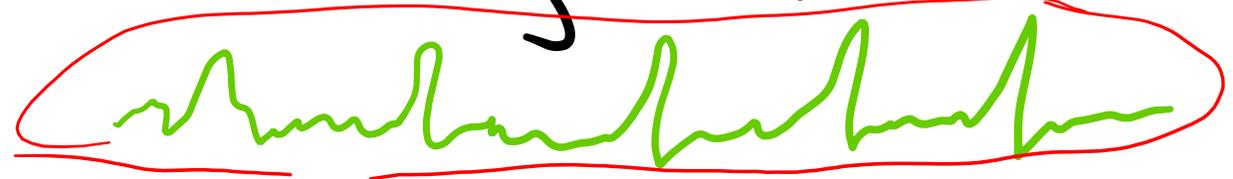

# Let's reject the common-mode with differential amplifiers:

In order to reject swings of  $V$  that occur on both the '+' and '-' lines of our signal – the so-called 'common mode.' Differential amplifiers are ideally suited to this purpose, as they only amplify differences between the signal leads. Let's take a look:

Start w/ Emitter Amps

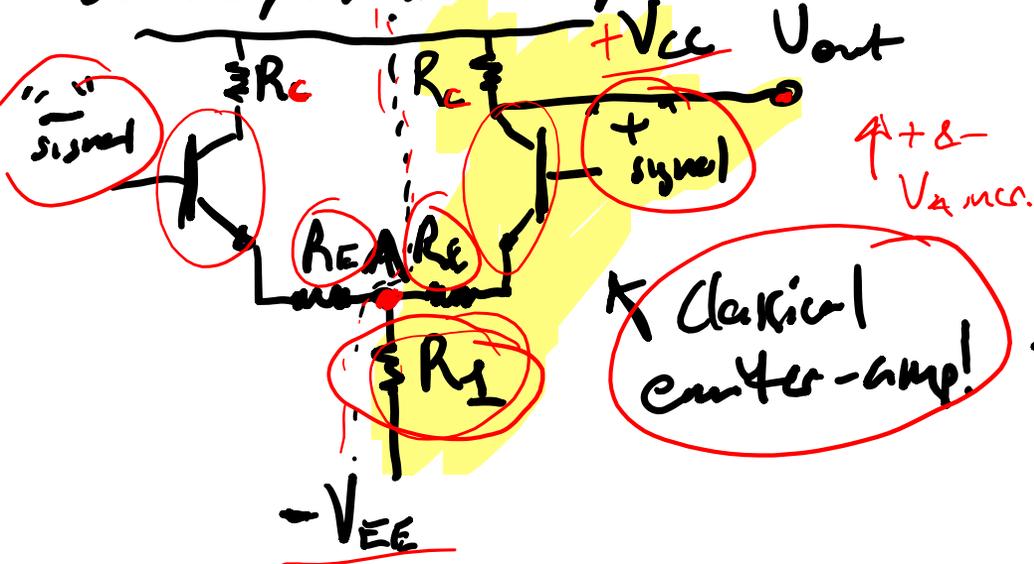

A is a quiescent point

How does this reject common-mode?

- Evaluate gain for "-" = "+" (common-mode)  
@ point A,  $V_A$  increases/decreases in proportion to input.

$$G_{cm} = \frac{R_C}{R_E + 2R_1}$$

- Evaluate gain for  $\Delta^- = -\Delta^+$  (normal-mode):  
@ point A,  $V$  is fixed (consider symmetry of circuit).

$$G_{nm} = \frac{-R_C}{2R_E}$$

from symmetry of V

# Differential amplifier continued:

Let us now evaluate the relative gain of CM & NM, the "CMRR" (common-mode rejection ratio):


$$\underline{\text{CMRR}} = \frac{G_{NM}}{G_{CM}} = \frac{R_C}{2R_E} \frac{(R_E + 2R_1)}{R_C} = \frac{R_E + 2R_1}{2R_E} \approx \left| \frac{R_1}{R_E} \right| \quad (\text{if } R_1 \gg R_E)$$

Points for discussion on Piazza:

1. Verify the gain of the common-mode with this amplifier construction
2. Verify the gain of the normal-mode with this amplifier construction
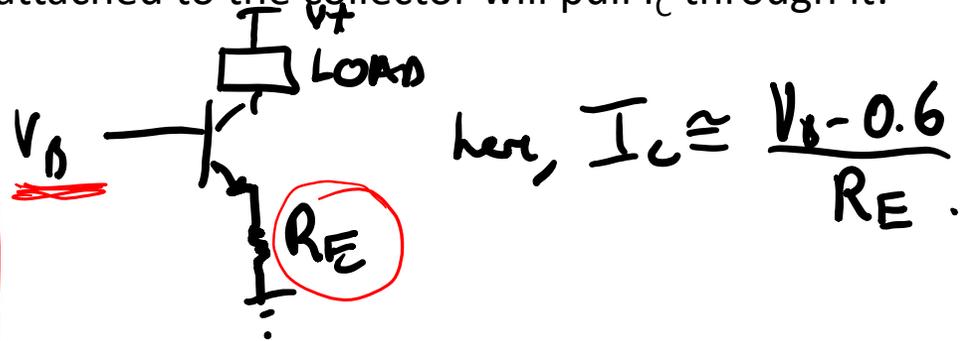
# Enhancing CMRR: current-source biasing

Note that for a given  $R_E$ , whatever load is attached to the collector will pull  $I_C$  through it:



This circuit is thus a current source.

Recognizing that point A in our differential amplifier is a quiescent point, what happens if we replace  $R_1$  with a current source? Let's review our CMRR:


$$CMRR = \frac{R_2}{R_E} \dots \text{but what is } R_2 \text{ for the current source?}$$

hint: for  $\Delta V$ , how does  $\Delta I$  change?

hint: for  $\Delta V$ , how does  $\Delta I$  change?

In any case,  $R_{eff}$  for the current source is large.

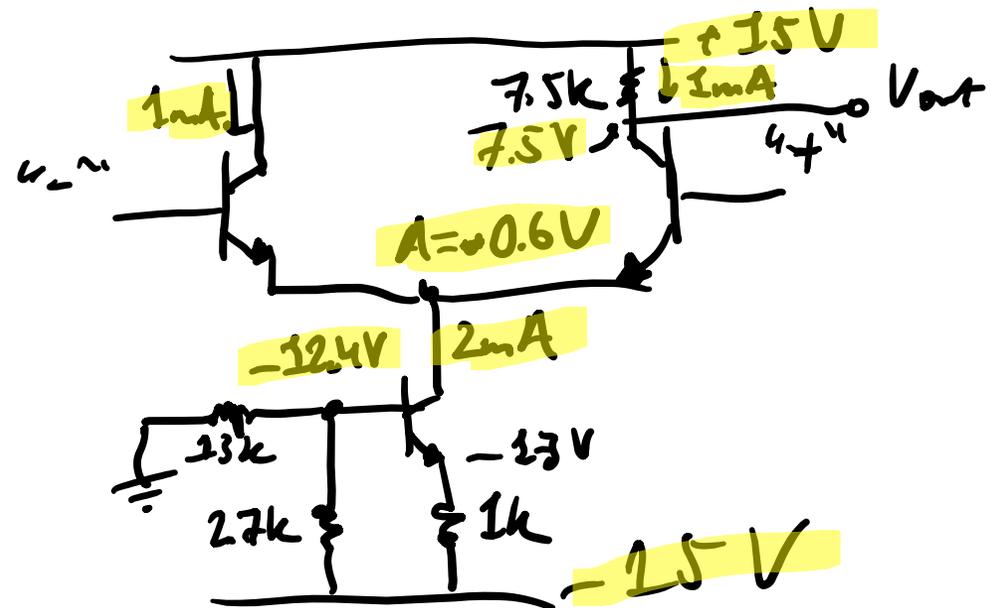- For a paired transistor set & a JFET current source, CMRR can exceed  $10^5$ !



# Building an open-loop op-amp from discretes

Here, we'll use discrete components to build an open-loop op-amp from discrete transistors & passives. Note that the layout prescribes the pins used on the CA 3096 IC, which includes 5 transistors on-board (3 npn & 2 pnp). These can offset T-related modifications to transistor response, as all transistors are the same temperature.

