
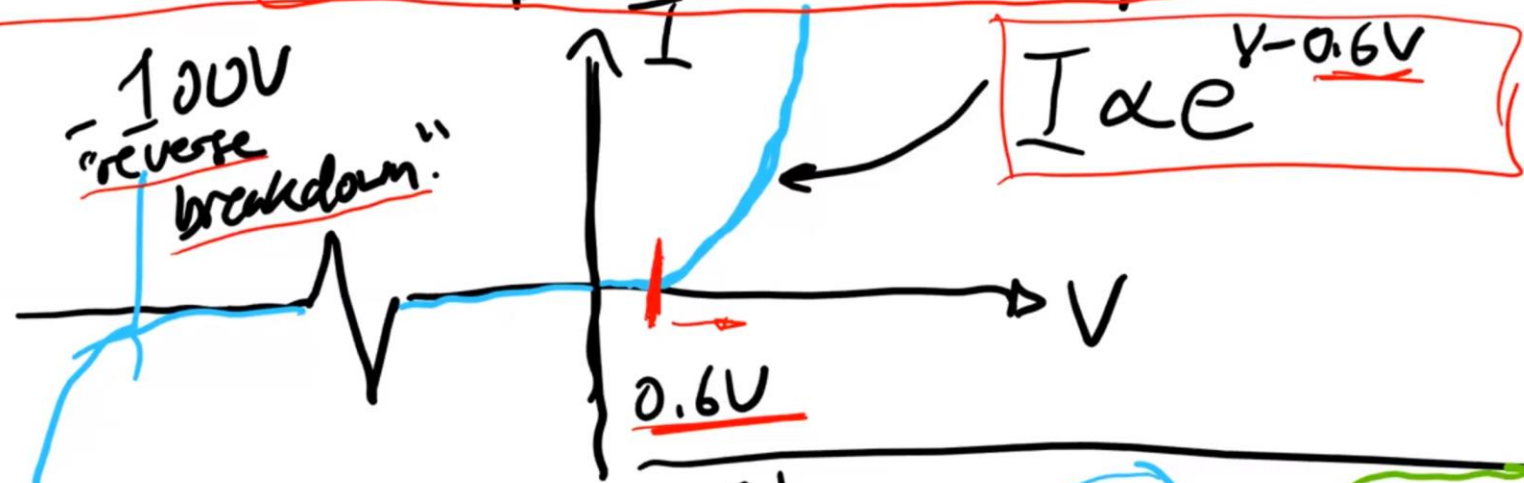


Active circuit elements: the transistor (**'transfer resistor'**)



And some useful circuits with transistors

A quick interlude on diodes...

Note: 0.6V "diode drop":

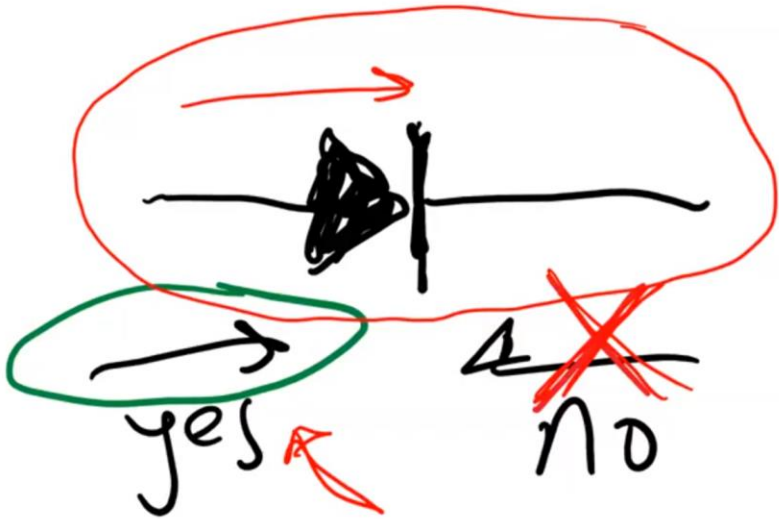


Devices: Rectifier:

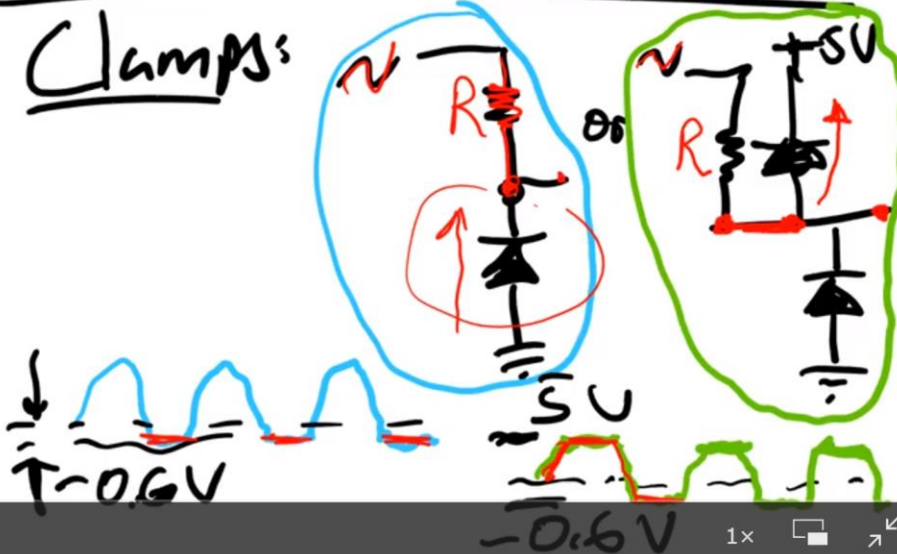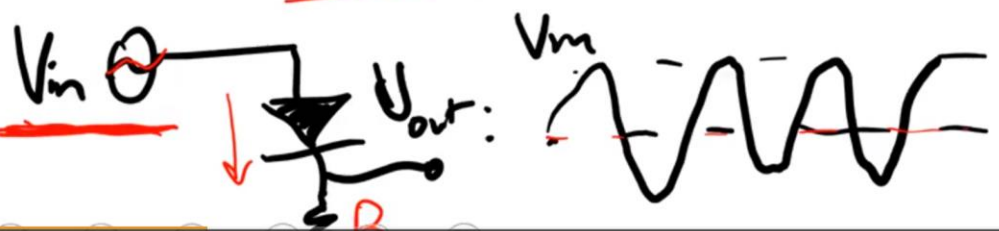


Onward with transistors: We'll work with BJTs (bipolar junction transistors)

Think of it like a valve:

valve

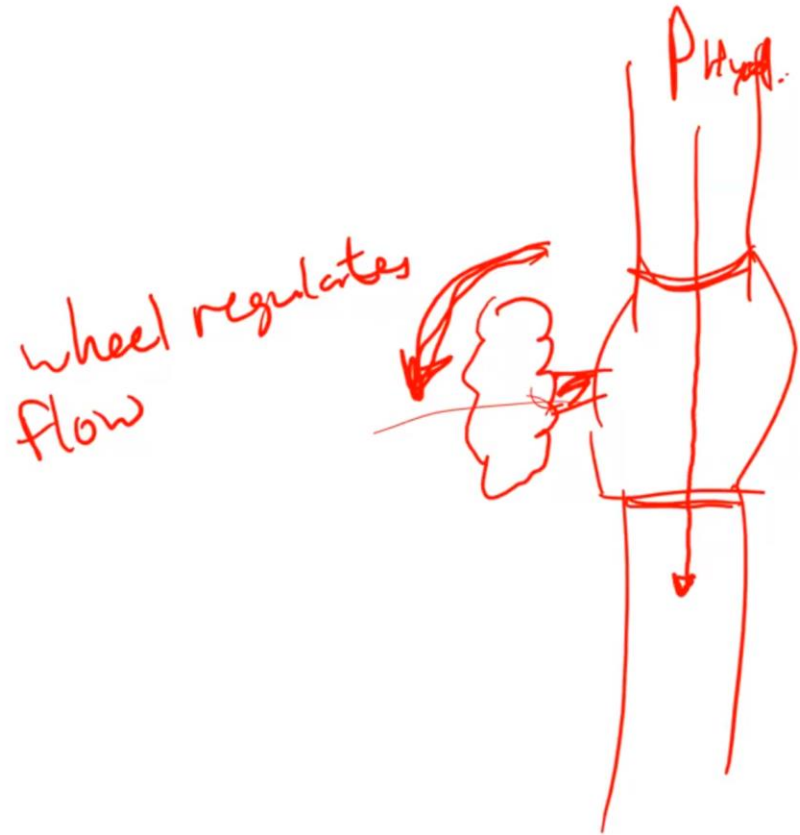


npn - transistor

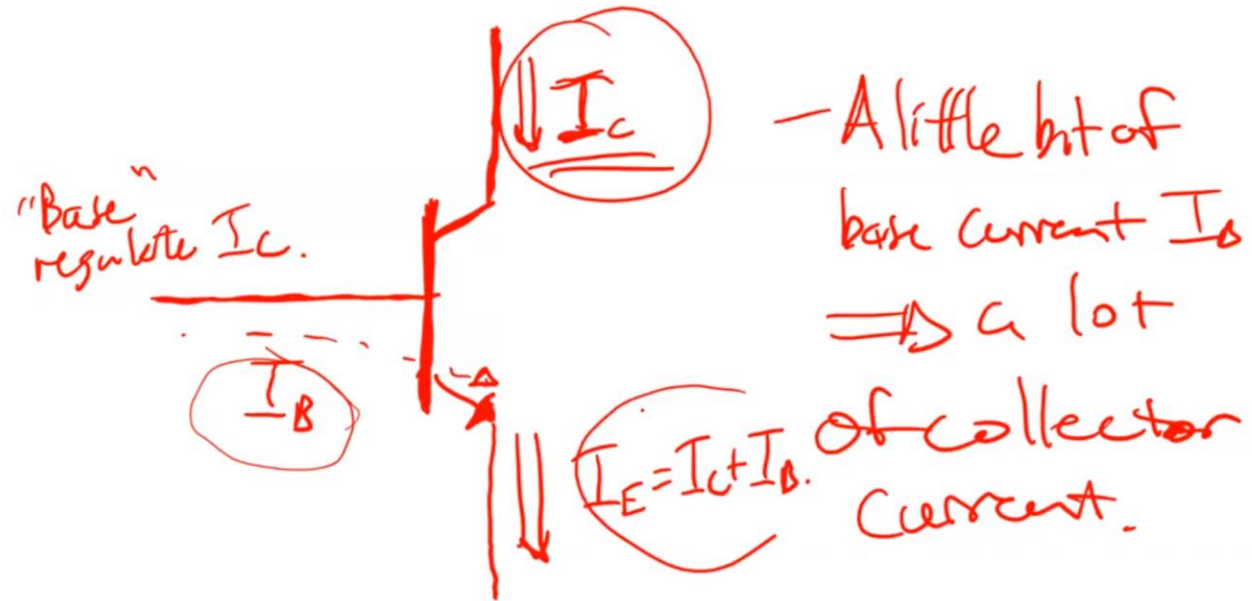

Some ground rules and two views of the transistor:

A relatively simple view: current amplifier

Current flows on transistor:

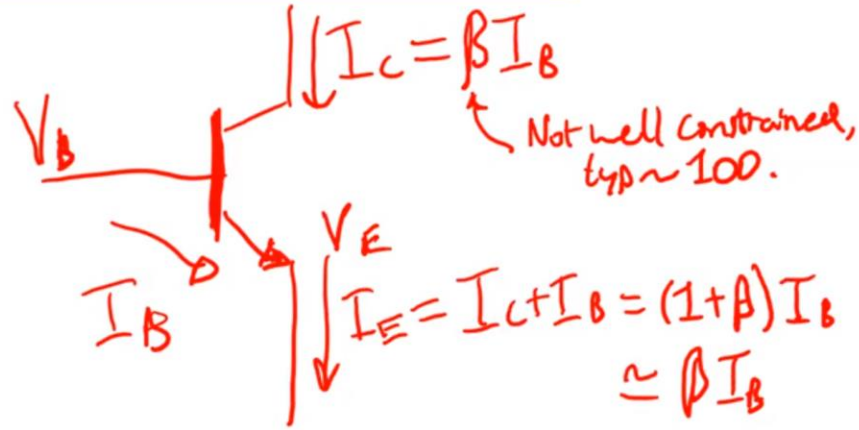

A simpler view: just assume β (aka h_{FE}) is at work

$$V_{BE} = \underline{0.6 V}$$

"Diode drop."

$$I_C \approx I_E$$


$\beta = I_C / I_B$

$$I_B \ll I_E$$

Ground rules:

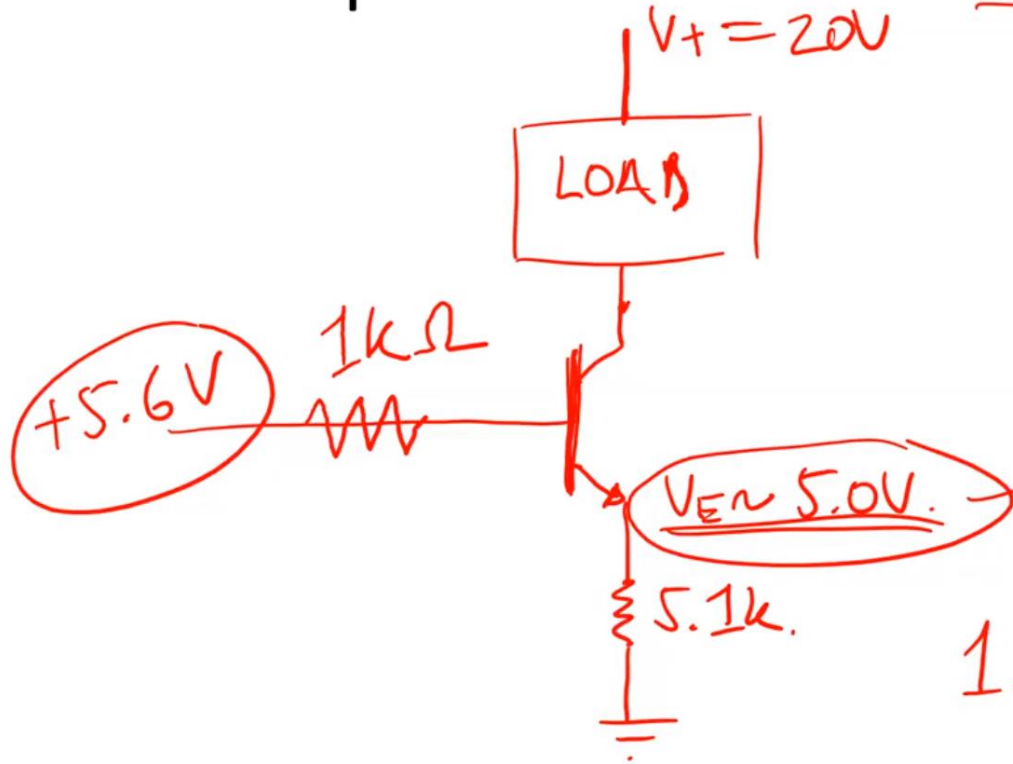1. $V_C > V_E$ by at least $\sim 0.1 V$
2. $V_B - V_E \approx 0.6 V$

Understanding transistor behavior through example circuits: a current source




$V_E = 5V, b, \text{Ohm: } 5 = I_E \cdot 5.1k.$
 $\Rightarrow I_E = \frac{5}{5.1k} \approx \underline{\underline{1mA}}$
 $\Rightarrow I_C \approx I_E.$

1. Let's say R_L is v. small: $R_L = 1k$:
 $V_C \approx 19V(?)$ $V_C > V_E$, Okay.

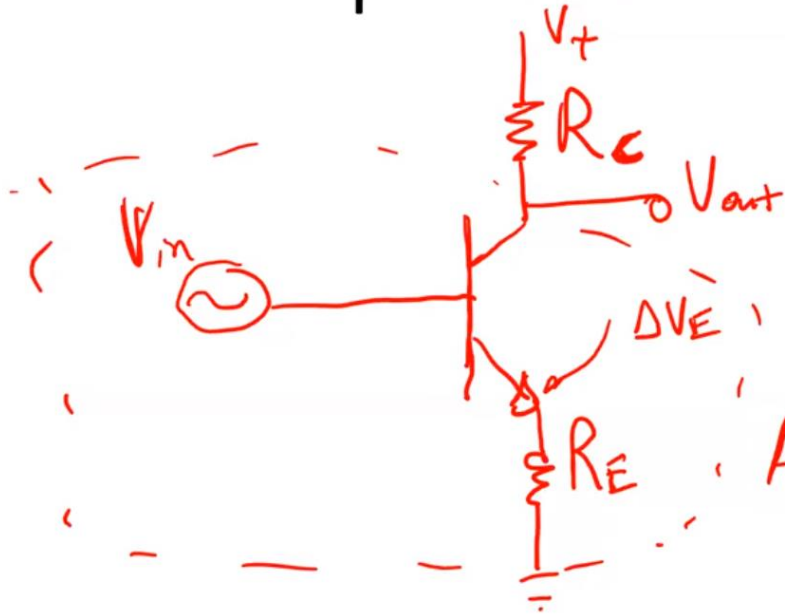2. R_L gets large: $100k$. $\Rightarrow V_+ \approx V_C \approx 1mA \cdot 100k \approx 100V (!)$

$\Rightarrow V_C \not\approx V_E \Rightarrow$ transistor behavior changes.
 effect is I_C is reduced.

Understanding transistor behavior through example circuits: *an emitter amplifier*




(1) Let $|V_{in}| = \Delta V_B$. (2) $\Delta V_B \rightarrow \Delta V_E$

$\Delta V_E \Rightarrow \Delta I_E \Rightarrow \Delta I_C$.


If R_E is small, we get a large ΔI_C .

Alternatively,

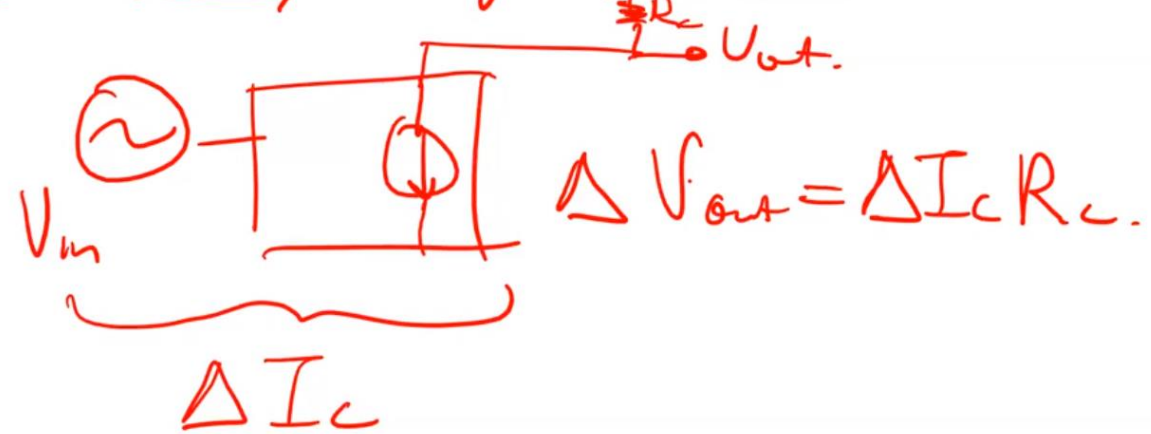

* Note: gain of emitter amp comes from $R_C > R_E$.

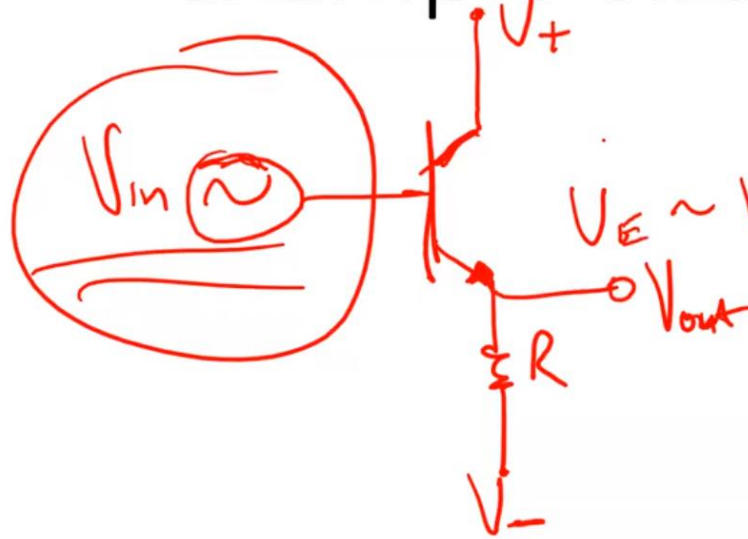Understanding transistor behavior through example circuits: *a follower*




$V_E \sim V_{in} (= V_{in} - 0.6)$.

Why would we do this?

- Incredible behavior of the transistor in changing impedances

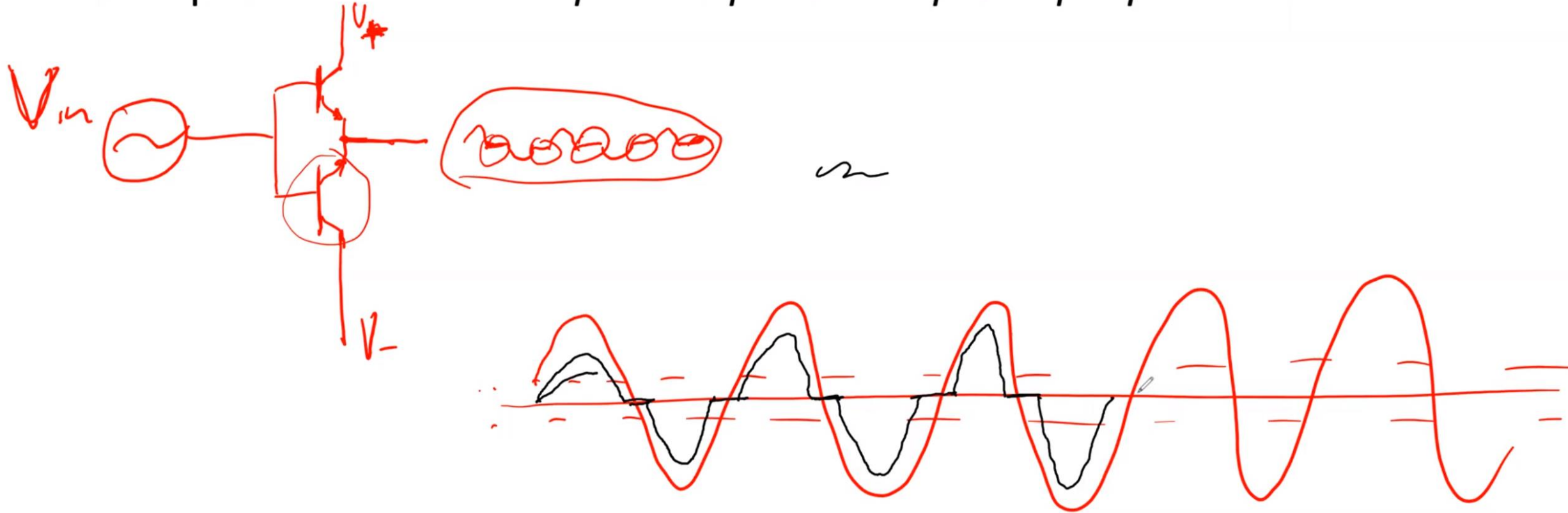Understanding transistor behavior through
example circuits: *a push-pull – npn - pnp device*




β is a poorly constrained parameter, around 100 but varies by 50-100%!!!

β – do *not* use it as a design parameter

Transistor impedance: *not* the V-divider view; 'rose-colored lens' effect

A second look at the follower:

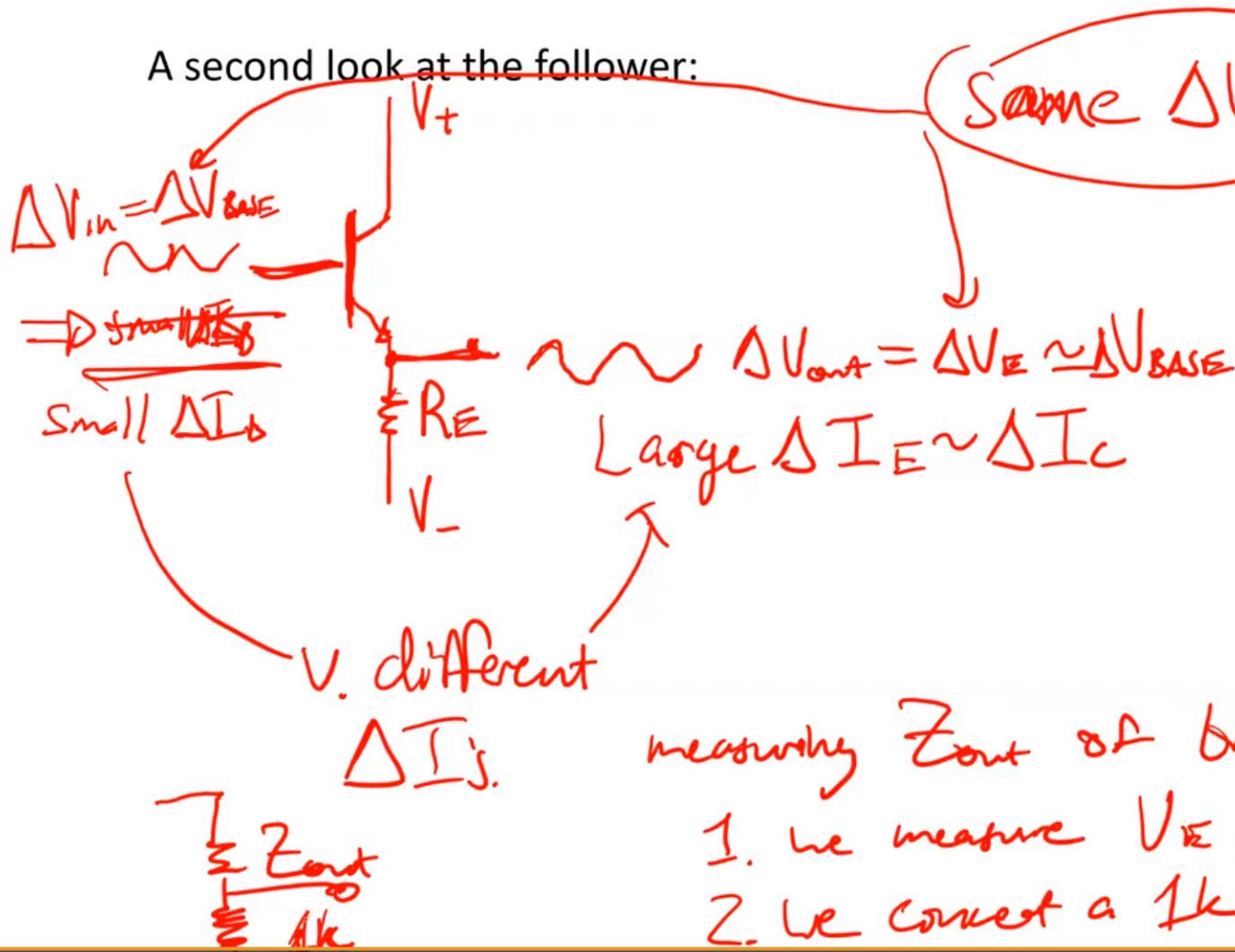

Same ΔV 's

* Looking into base of the transistor, I see a v. large impedance.

* Look into the emitter from output, we see a v. low impedance.

measuring Z_{out} of transistor:

1. we measure V_E w/out load, with $\approx 33k$ on base
2. we connect a $1k$ load to ground; measure ΔV_E again

Asymmetry introduces clipping*


(can also be seen for a single-supply follower driven with a symmetric input)

Remark on biasing:



$|V_m| = 5V$

"A/C coupling"

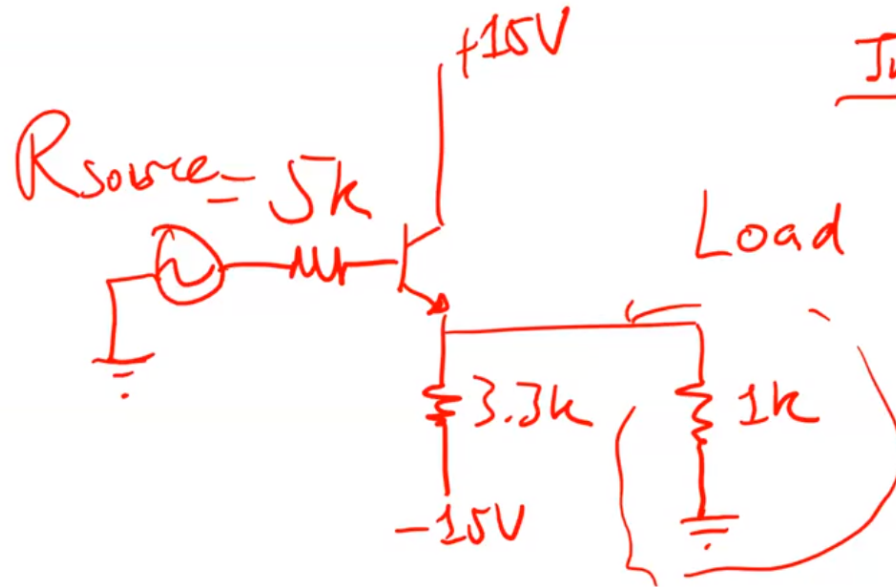

Input impedance:

$$R_{in} \sim \beta(R_E || R_L) \sim 50k$$

$$R_{in} \sim 10 \times R_{source}$$



$R_{th} = 0.75k$
 $V_{th} = -3.5V$
 \Rightarrow clipping.

Output impedance:


looks like $R_E || \frac{R_{source}}{\beta} \sim 50\Omega \approx 50\Omega \Rightarrow R_{out} \sim \frac{R_L}{20}$

Again, no dropout.

At V_m as low as possible, transistor shuts off. $\Rightarrow 3.3k$ & $1k$ \downarrow

* Read ch 2 of
AoE. up through § 2.2.7.

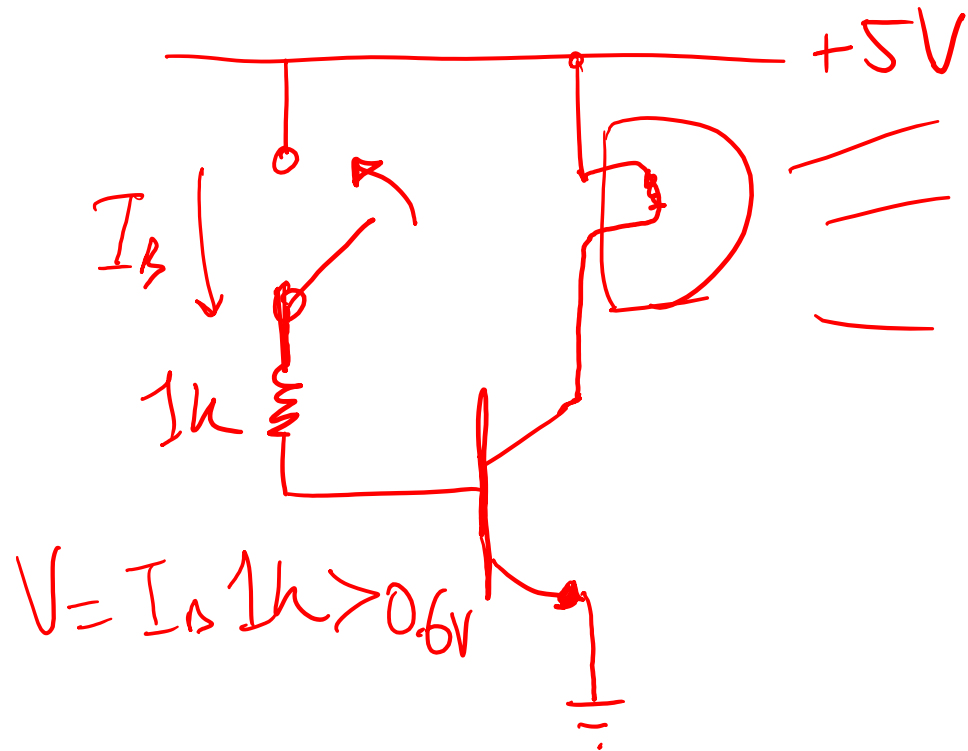An anomalous transistor circuit: the switch



- Transistor is in one of two states:


1. Totally on \rightarrow
current passes through
lamp, lightens it.

2. Totally off: \rightarrow
No current through lamp
no light.


$I_C \neq \beta I_B$; V_{CE} is low reducing
power consumed by transistor.

A summary of our transistor circuits:


Follower

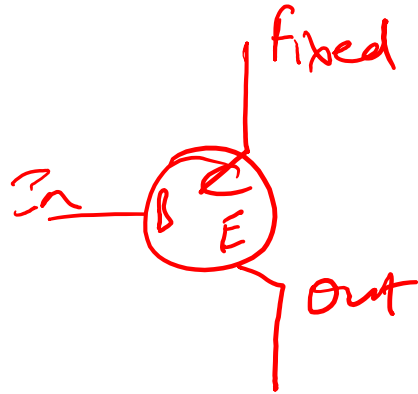

Current source

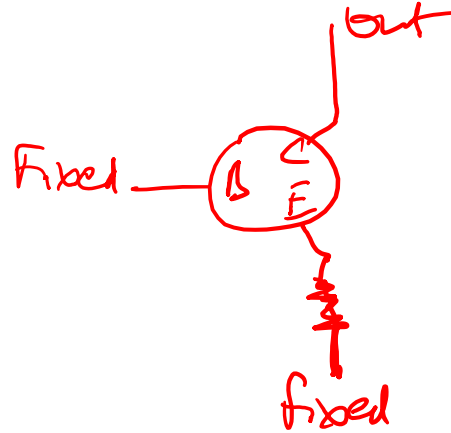

Amplifier

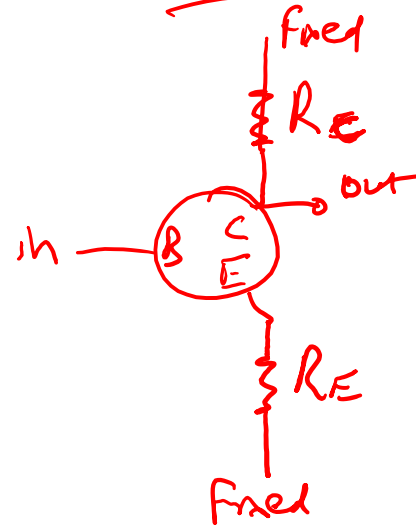

Switch

