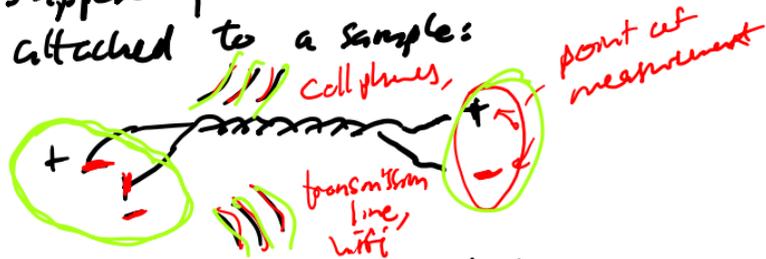


# Active circuit elements: the transistor (**transfer resistor**) and the op-amp

And some useful circuits with transistors & amplifiers

The dreaded *common-mode*: how to handle a signal that is susceptible to ambient electrical noise?

Suppose you have a transducer attached to a sample:




And there is ambient electrical noise:

Note that both leads,  $+ \Delta -$  carry this noise!

- you can easily see this from the 50 Hz signal carried on power lines.

Often, your signal will look like this:

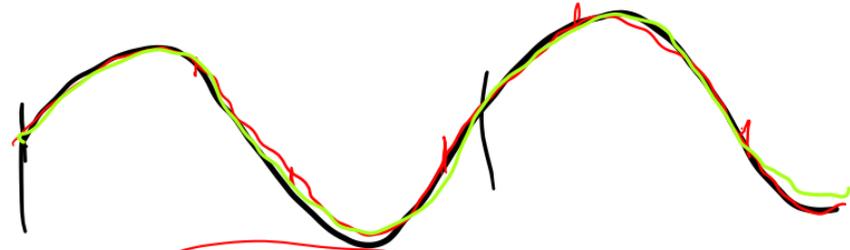


$$\Delta T = \frac{1}{50}$$

While expecting this: ✓



# The 'ideal amplifier:'

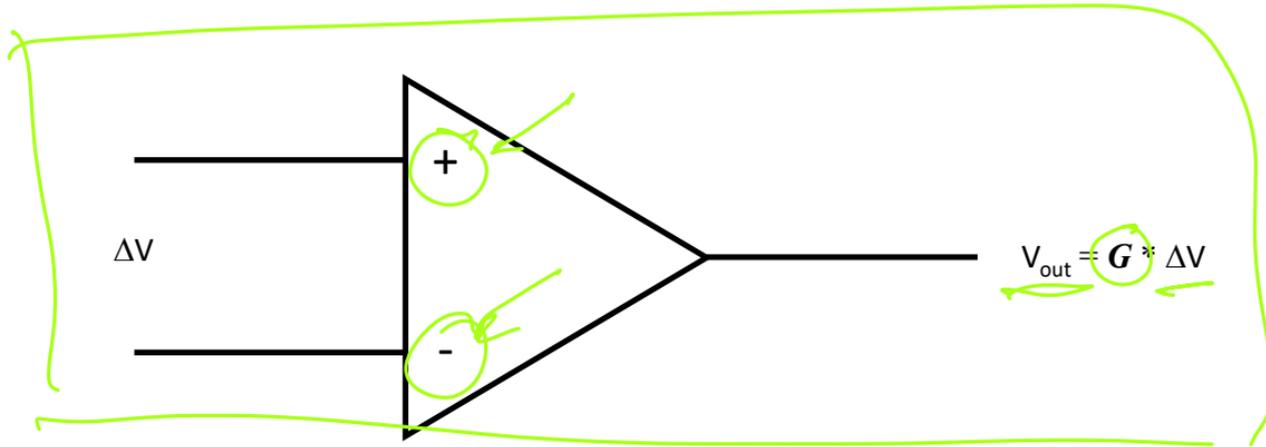


- Gain,  $G$  can be arbitrary, and very large if needed
- Bandwidth is infinite
- No load on the input signal (infinite input impedance)
- Perfect rejection of common-mode
- Perfect rejection of power-supply noise

Clearly, we cannot get all of these things in one...

But we can get close!
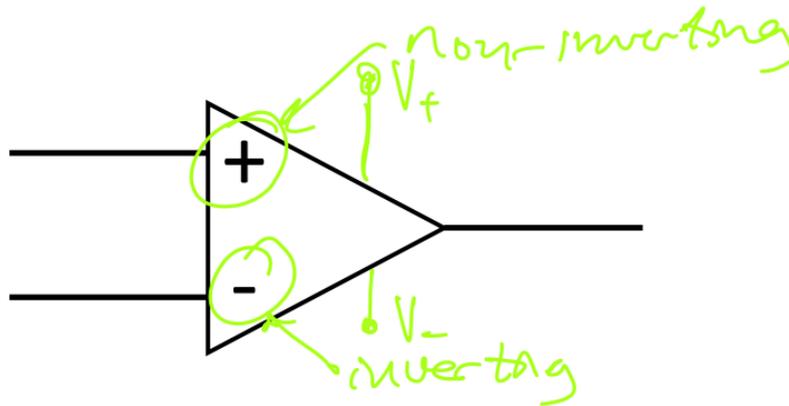
# Enter *the op-amp*:

An op-amp is a very high-gain\* dc-coupled differential amplifier with a single-ended output.





\* The typical op-amp (e.g. the LF411) has an open-loop gain of  $10^5 - 10^6$

Why would we call the non-inverting input *the non-inverting input*? Isn't it much easier just to call it the 'positive input'?  
How many leads would be necessary for such an amplifier?



How is such an amazing device constructed? => transistors!

# A quick interlude on diodes...

Note: 0.6V "diode drop":

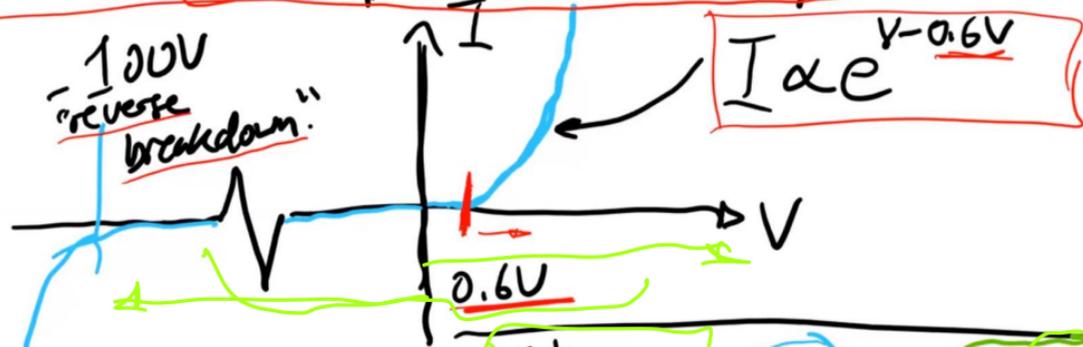
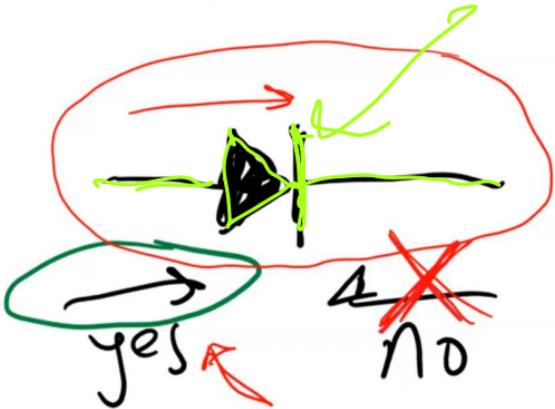


Devices: Rectifier:

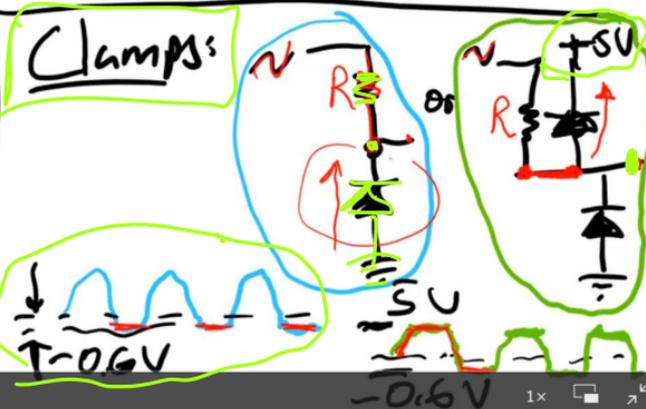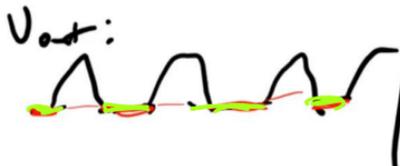


# Onward with transistors: We'll work with BJTs (bipolar junction transistors)

Think of it like a valve:

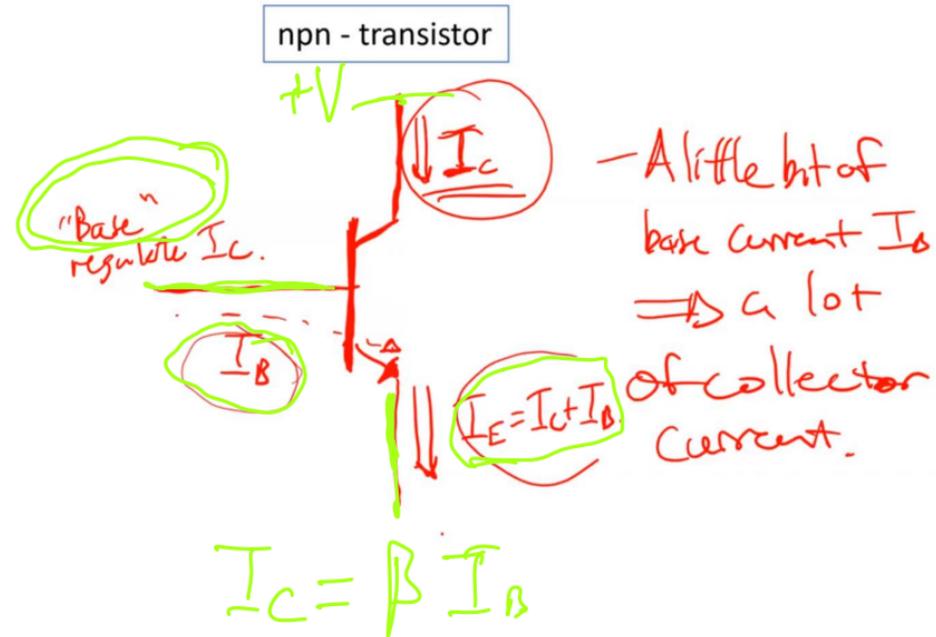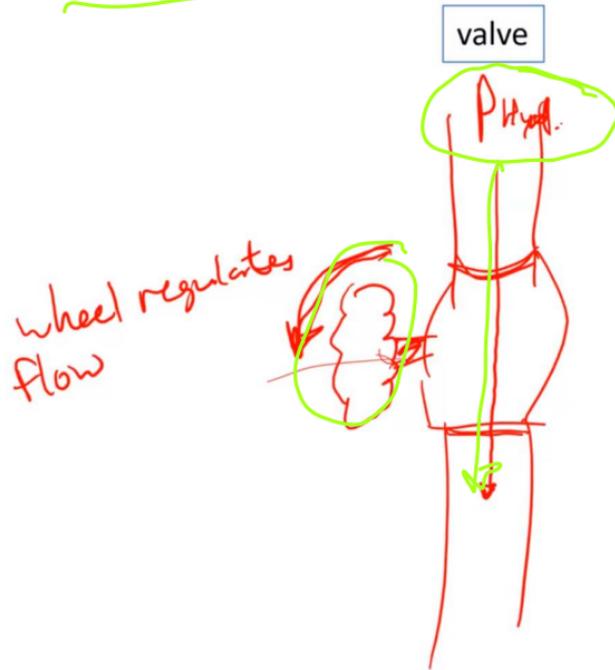
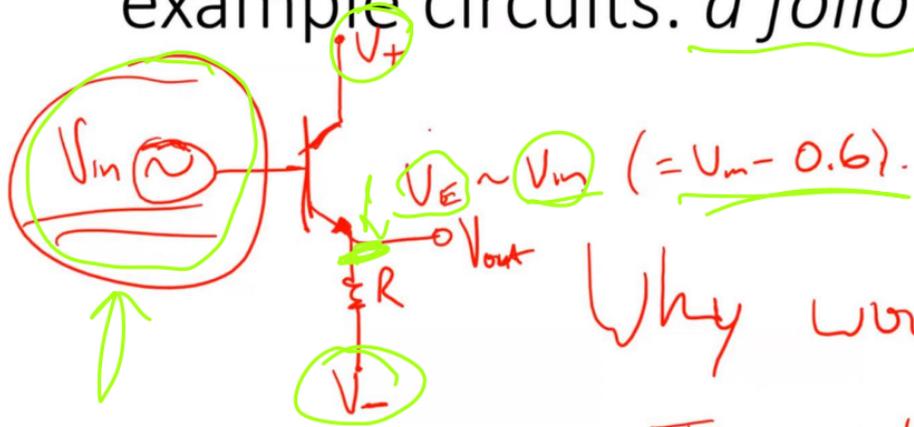
# Understanding transistor behavior through example circuits: a follower




Why would we do this?

- Incredible behavior of the transistor in changing impedances

# Transistor impedance: *not* the V-divider view; 'rose-colored lens' effect

A second look at the follower:

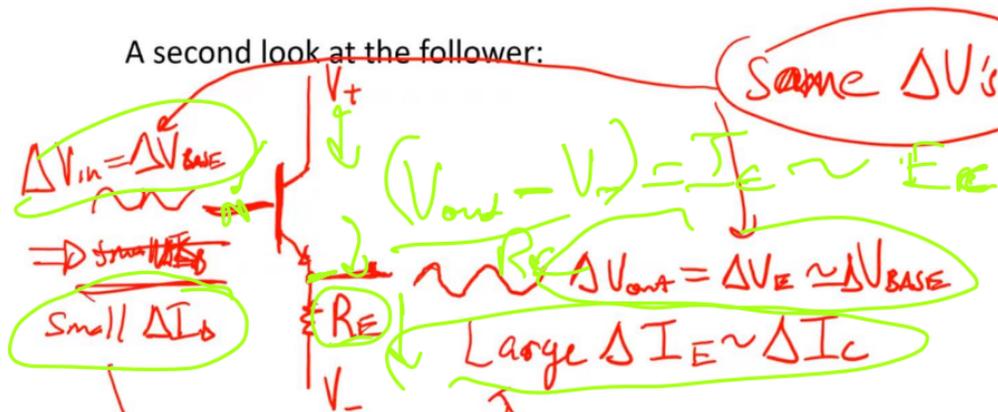

\* Looking into base of the transistor, I see a v. large impedance.

\* Look into the emitter from output, we see a v. low impedance.


v. different  $\Delta I$ 's

measuring  $Z_{out}$  of transistor.

1. we measure  $V_E$  w/out load, with  $\approx 33k$  on base
2. we connect a  $1k$  load to ground; measure  $\Delta V_{E,osc}$




# A summary of our transistor circuits:

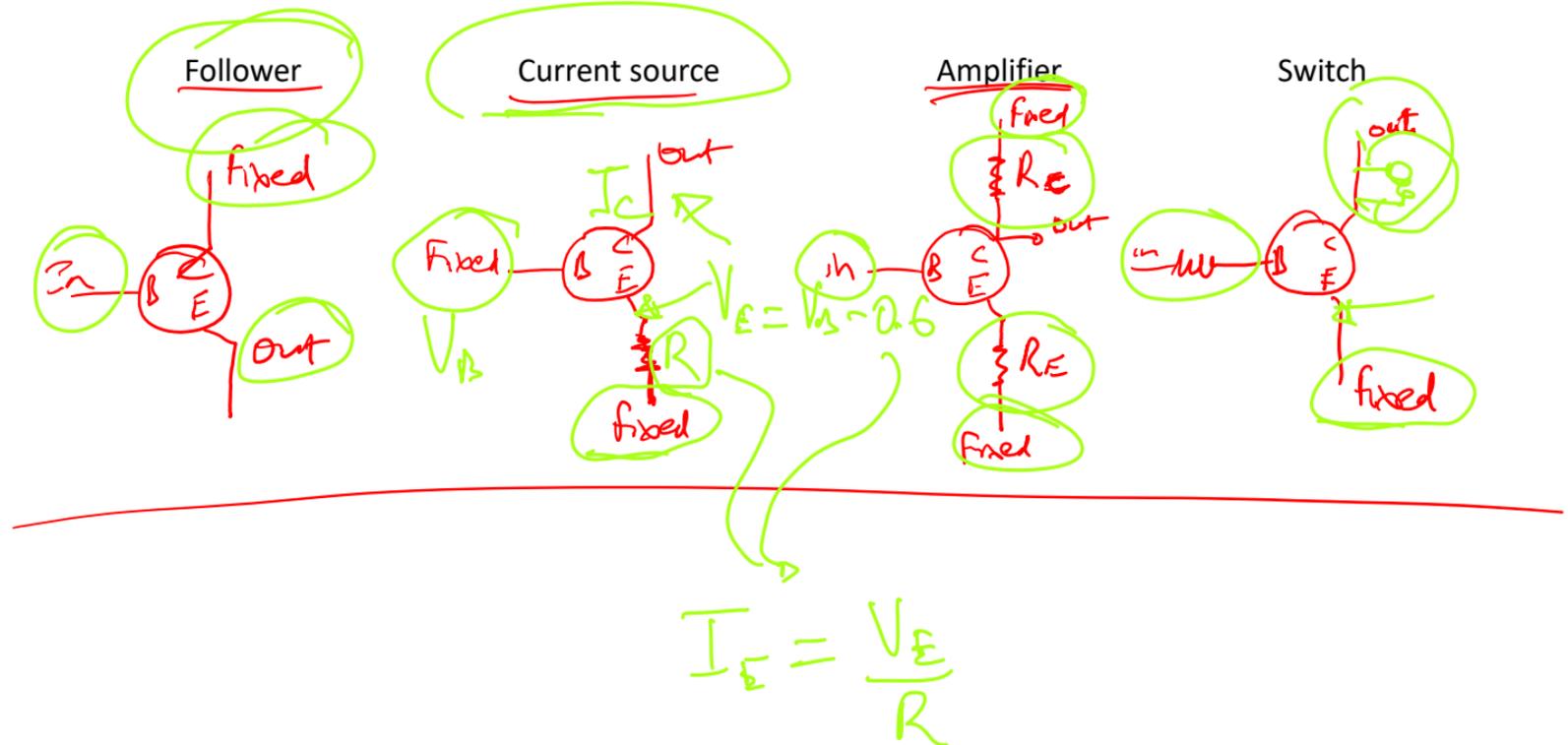
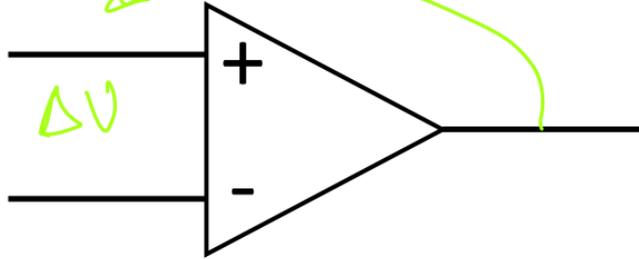
# Back to *the op-amp*:

An op-amp is a very high-gain\* dc-coupled differential amplifier with a single-ended output.




The 'golden rules' for op-amp behavior assuming it is operating with negative feedback

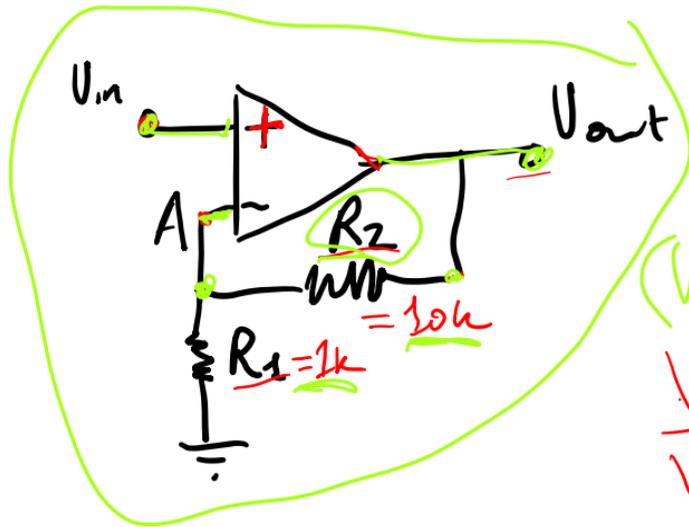- I. The output ***attempts to do*** whatever is necessary to make the ***voltage difference between the inputs 0***.
- II. The inputs draw no current.

Can the op-amp dictate the voltage at the inputs? Why or why not?

A typical op-amp non-inverting amplifier – operating with negative feedback:



- From GRI,  $V_A = V_{in}$
- But,  $V_A$  comes from a V-divider:

$$(V_{in} =) V_A = \frac{V_{out} R_2}{R_1 + R_2} \quad \left. \vphantom{V_A} \right\} \text{this is our gain!}$$

$$\frac{V_{out}}{V_{in}} = \underline{G} = \frac{R_1 + R_2}{R_1} = \boxed{1 + \frac{R_2}{R_1}}$$

$$G = 1 + \frac{10k}{1k} = 11.$$

# Turn it up to 11!

## *A note on negative feedback*

Today, we'll build an amplifier using the LF411 op-amp with a gain of about **10**. Recall that op-amps have enormous open-loop gain ... why would we want to throw away all of the amazing open-loop gain?


Indeed, we do 'throw away' gain - but not without redeeming merit! Keep in mind, we now have *feedback* in our circuit. This is the key advantage. When the open-loop gain vastly exceeds the gain attained via feedback, we refer to this as *negative feedback* – not like a news-cycle, where bad news begets bad news (this is *positive* feedback by our definition. If you're not confused, just wait a moment...)

Negative feedback essentially consists of throwing away the 'bad' while keeping the 'good.' The output of the amplifier is attenuated, and compared with another input to the amplifier, and the *deviation from the input* then 'directs' the amplifier to move in the correct direction – thus suppressing noise, for example.

Consider an amplifier without feedback – any time it is exposed to noise, that noise is also amplified, and can drive the output ***away from*** the intended ' $G \cdot \Delta V$ ' behavior.

# Basic op-amp circuits & their analysis

An op-amp follower:

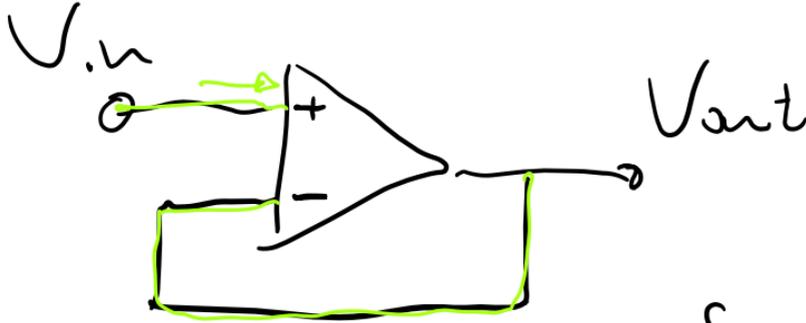

Also called a buffer.


What is the benefit of this circuit – e.g. why would one want to use it?

1.  $V_{in}$  increases
2.  $\Delta V_{+}$  increases
3. Amp drives output up until  $V_{out} = V_{in}$ .

Simple! At step 3, both Golden Rules apply – first GR I: the output responds to  $\Delta V_{+}$ ; second, GR II:  $V_{-} = V_{out}$ .

# Basic op-amp circuits & their analysis

Inverting amplifier:

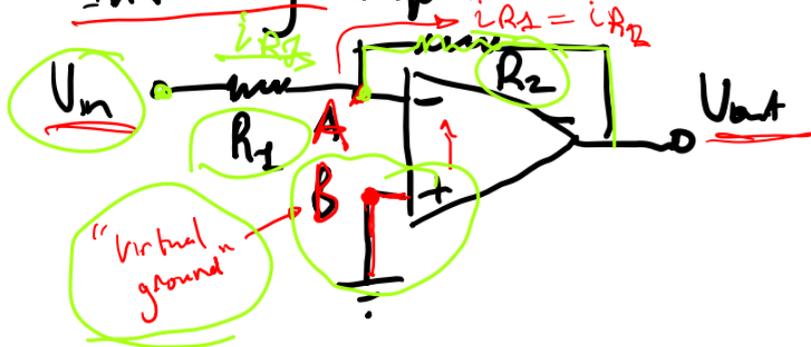

→ Point B is a "virtual ground".

GRI: Point A is also at  $V=0$ .

•  $\Delta V_{in-A} = I_{R1} \cdot R_1 = V_{in}$

• GRII:  $I_{R1} = I_{R2} = I$

$\Rightarrow \Delta V_{o-A} = I \cdot R_2 = V_{out}$

Thus,  $\frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1} = G$ .


Note: gain is negative here: if  $V_{in} > 0$ ,  $V_{out} < 0$ .

What is the input impedance of this amplifier? (hint: it is not the input impedance of the op-amp!)

# Basic op-amp circuits & their analysis

## Current sources:

A basic design, with a glaring problem:

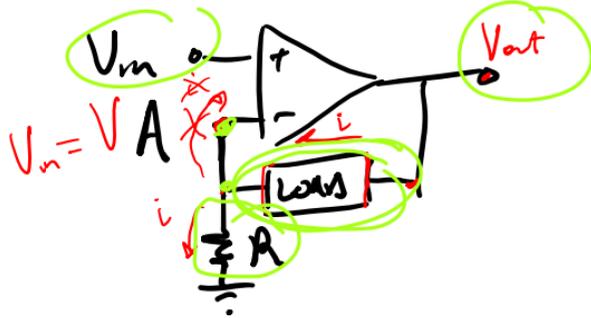


GRI:  $V_A = V_{IN}$ ; Thus, by GRII,  $I = \frac{V_m}{R}$

•  $I$  passes through the load.

What is the 'glaring problem' with this design? E.g. Why might it not be ideal for use in pushing a current through a resistive load?

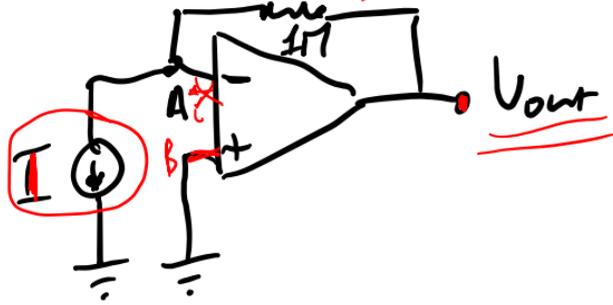
# Basic op-amp circuits & their analysis

An ideal current-to-voltage converter (a "trans-impedance" amp)



This circuit produces an output of  $1V/\mu A$  of current: useful for e.g. a photodiode, which makes current when exposed to light.

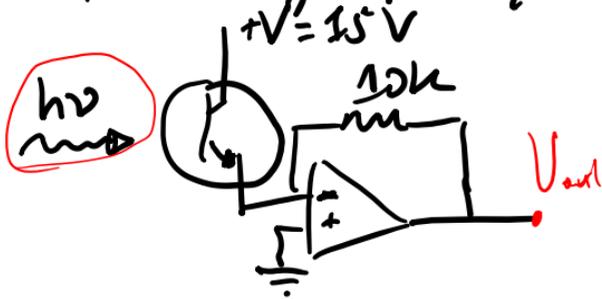Alternatively, suppose your current source requires power:



for e.g. a PMT

The devices we've review thus far do not constitute a comprehensive list of useful op-amp circuits. Find another circuit that uses negative feedback to do something useful!

# Cautionary notes for application of the GRs

- Golden rules only apply if the op-amp is in the 'active region' (i.e. not saturated at  $V_+$  or  $V_-$  of the supply)
- Feedback *must be negative* – be careful not to mix up the inverting and non-inverting inputs
- There must always be feedback at DC – otherwise, you're guaranteed to saturate. Alternatively, apply a high-pass filter to the input to eliminate concerns about DC offset driving the amp into saturation.
- Beware the maximum differential input voltage – if overdriven, the amp can fail catastrophically.