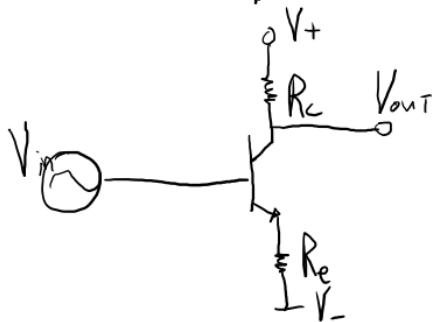


Day 3: Differential amplifiers to op-amps

A transistor amplifier:



How does this work?

1. V_{in} controls V_e , changing emitter current.

$$I_e = \frac{V_{in} - V_-}{R_E}$$

2. Due to the large current gain of transistor (β), the current drawn from V_+ through R_C :

$$I_c = \frac{V_+ - V_{out}}{R_C} \Rightarrow V_{out}$$


$$\text{Gain: } G = \frac{V_{out}}{V_{in}} \approx \frac{I_c R_C}{I_e R_E} \approx \frac{R_C}{R_E}$$

Often we are more interested in a voltage difference than voltage signal.



How do we build such an amplifier?

Use 2 transistors!

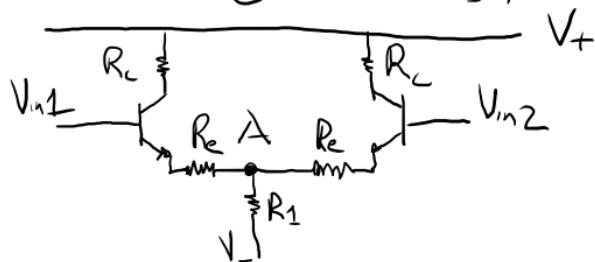


Suppose both V_{m1} & V_{m2} are the same.

- The voltage at A will vary with the applied voltage @ V_{m1} & V_{m2} "common-mode"

Then we can calculate the gain: $G_{cm} = \frac{R_c}{(R_E + 2R_{\pi})}$

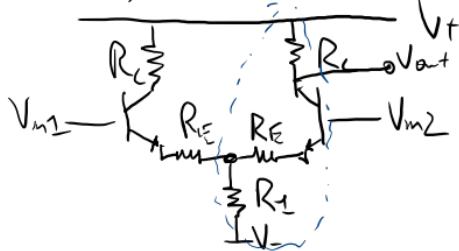Now consider the case signal, $V_{m2} = -V_{m1}$



where we apply a perfectly asymmetric signal. What is the voltage at point A? 0! by symmetry. Both AUs cancel out.

What is the gain?
"Differential"


$$G_{\text{diff}} = \frac{R_L}{2R_E} \rightarrow \text{From symmetry of voltage fluctuation.}$$

How well does this amp reject the common mode?

$$\frac{G_{\text{diff}}}{G_{\text{CM}}} = \frac{R_L}{2R_E} \frac{(R_E + 2R_1)}{R_L} \simeq \left(\frac{R_1}{R_E} \right) \text{ when } R_1 \gg R_E$$

↳ "Common mode rejection ratio" CMRR.

On to op-amps:

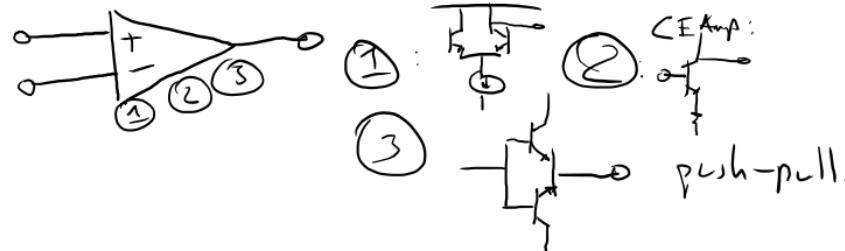

Op-amps have a lot of gain.
They use negative feedback to obtain incredible
consistent performance.

Why negative feedback?

- Build in an excess of gain: feed out signal
into the inputs so as to cancel the
excess gain & stabilize the op-amp's performance.


Feedback will close the loop unlike an transistor
amplifiers, which are open-loop.

The excess gain is enormous. Open-loop gain of LF411
is typically 200,000.

"Golden rules" for op-amp operation:

1. The output does whatever it can to make the voltage difference at one input 0.
 2. The inputs draw no current
↳ Supply is different: V_+ , V_- .
must be powered to work.
- n.b. these rules only apply when op-amp is used with negative feedback.

* A follower :

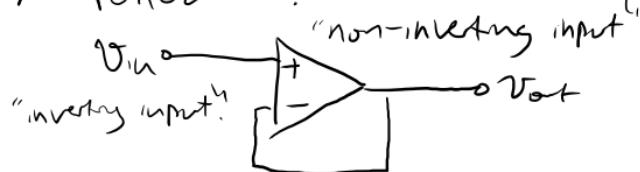

estimate: what is the input impedance, R_{in} ?

What is the voltage offset: $V_{out} - V_{in}$?


I convert to emitter follower.

What is the output impedance, R_{out} ?



① Apply $\Delta v \downarrow$
② High-gain open-loop causes the
charge (all feedback loop,
and for enormous current
sources)

* Non-inverting amplifier.

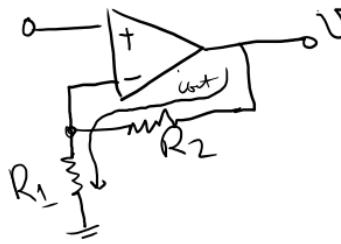

Just what is the gain of this amplifier?

- Apply 1V to "+" input:

$$\text{Input } V = 1V.$$

- Current to ground is $\frac{1V}{R_1}$

- $\frac{V_{out} - 1V}{R_2} = \frac{1V}{R_1}$


$$\therefore V_{out} = 1 + \frac{R_2}{R_1} \quad G = 1 + \frac{R_2}{R_1}$$

- Amplifier when $R_2 > R_1$.

- What is R_{in} ? ∞ .

- What is R_{out} ? very low (~ 0).

* Inverting amplifier

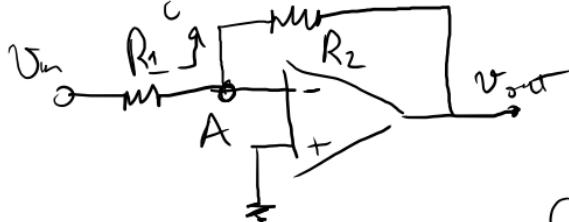

Apply 1V @ input.
What is V_A ? ($0V, \infty$)
"Virtual ground".

Current is $\frac{1V}{R_1}$.


Thus current also goes through R_2 :

$$V_{out} = i \cdot R_2 = \frac{1V \cdot R_2}{R_1} = \frac{R_2}{R_1}$$


$$G = \frac{V_{out}}{V_{in}} = \frac{R_2}{R_1}$$

* What is R_m ? ~~R_2~~ . It's not "huge". In fact, R_1 ...

* Current Source:

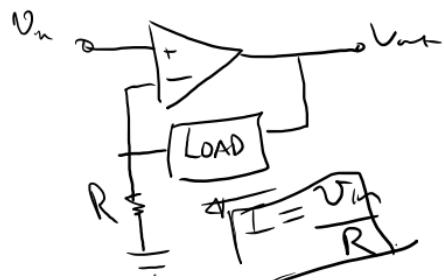

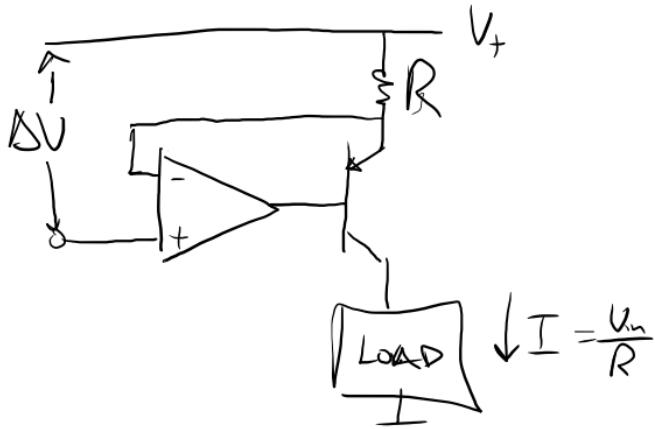not a real current source, b/c V_{in} @ inverting input is not 0.



Op amp improves transient behavior.
The load is connected to ground.

* Schmitt Trigger: Very stable switch, where switch is set programmably.

* Trans-impedance amplifier: Amplifies current sources.

* Integrates & differentiates, filters etc