


Today:

- Bridge Amplifier circuit for load cells.
(Load cell)
→ "Instrumentation amplifier"

- Considerations for measuring junction resistance.
 - Use Talbot! to estimate R_{junction} .
 - Feasible plan for measurement: Current source + Amp.
 - Low-level measurements handbook. (Keithley)
ch. 3 low- R measurements.
 - compare measurement w/ HZ theory.
-


Strain gauges & load cells: LC's typ circuit of 4 resistors:
(Strain gauges):

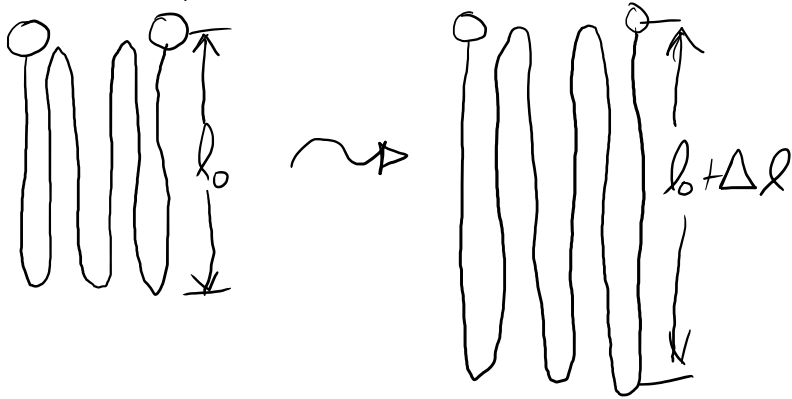Strain gauges : precision resistors made of thin metallic film:



Increasing the length increases its resistance.


Wheatstone Bridge:

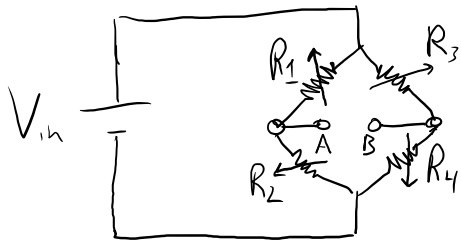

Thermal effects on R are automatically compensated:

Typ. $R_1 = R_2 = R_3 = R_4$ when unloaded.

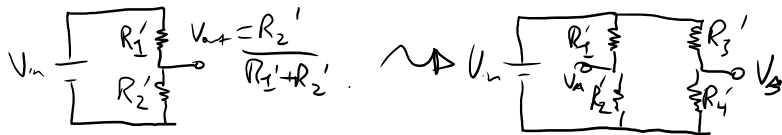When unloaded: $V_A = V_B = V_{in}/2$. (hence mA. Amp).



$$V_A = \frac{R_2'}{R_1' + R_2'} \cdot V_{in} \quad \& \quad V_B = \frac{R_4'}{R_3' + R_4'} \cdot V_{in} \quad (\text{unloaded all } R_i \text{ same} \Rightarrow V_A = V_B)$$

The bridge is laid out so that

R_1' & R_2' ; R_3' & R_4' are loaded opposite.

R_1' in tension $\Rightarrow R_2'$ in compression $\Rightarrow R_2'$ & R_3' ; R_3' & R_4' are opposite as well.

Start building instrumentation amp to amplify load cell. (INA...)

- Build current source & calibrate it (Ref 102 & datasheet)
 - V amp & calibrate that.
- After estimation!

- Beware thermoelectric potential.

Tuesdays (next Tues) we're open 16-19..